

Team Name:

Date:

Scenario 1

How could you light up three 1V light bulbs using three 1.5V batteries?

(Show diagrams and calculations for both series and parallel circuits.)

Scenario 1

Which will last longer to power a circuit, two AA batteries in series or 4 AAA batteries in parallel?

(Show diagrams and calculations for both series and parallel circuits.)